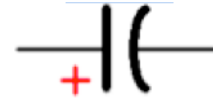


Semester 1 Final (Unit 1.1-2.4)

Multiple Choice: Circle the choice that best answers the question.

- What tool is used to measure multiple electrical related values?
 - Ammeter
 - Ampmeter
 - Digital Multi-Meter
 - Voltmeter
- Capacitors are used to
 - Add resistance to a circuit
 - Determine voltage level
 - Store electrical charge
 - Cap current levels
- Which is NOT a type of capacitor
 - Ceramic
 - Electrolytic
 - Mylar
 - Plastic
- What does LED stand for
 - Light electric display
 - Light emitting diode
 - Large enhanced display
 - Large electric display
- Which is NOT a type of integrated circuit package
 - BGCC
 - DIP
 - PLCC
 - SOIC
- A resistor value with colors (Red, Blue, Green, Gold) is
 - 265 +/-5%
 - 26k +/-5%
 - 260k +/-5%
 - 2.6M +/- 5%

- What does the following schematic represent



- Battery
 - Ceramic Capacitor
 - Carbon Resistor
 - Electrolytic Capacitor
- What does the following schematic represent



- Battery
 - Ceramic Capacitor
 - Resistor
 - LED
- Resistance is measured in units of
 - Amps
 - Farads
 - Ohms
 - Volts

- What is the following object?



- Battery
 - Capacitor
 - Resistor
 - LED
- What type of capacitor is shown below



- Ceramic
- Axial Electrolytic
- Radial Electrolytic
- Mylar

12. What is the value of the capacitor shown below




- a. 252 pf +/- 10%
 - b. 252 f -20%, +50%
 - c. 2500 f +/- 10%
 - d. 2500 pf -20%, +50%
13. When working with electricity or electrical components you should
- a. Keep areas clear of liquids
 - b. Not wear jewelry
 - c. Assume all circuits are on
 - d. Label damaged equipment
 - e. All of the above
14. Which type of fire extinguisher should you NOT use when working with electronics?
- a. Type A
 - b. Type B
 - c. Type C
 - d. Type D
15. At what threshold does current become deadly?
- a. 10 A
 - b. 1 A
 - c. 100 mA
 - d. 1 mA
16. The following element in solder can be dangerous to your health.
- a. Tin
 - b. Copper
 - c. Lead
 - d. Silver
17. To remove excess solder off of the soldering iron you should
- a. Tap the soldering iron in the table
 - b. Rub it off with your hand
 - c. Wipe it off on a wet sponge
 - d. Wipe it off on your shirt

18. Which of the following is in scientific notation

- a. 112,000
 - b. 1.0006×10^{-2}
 - c. 564×10^3
 - d. 127
19. Pico means
- a. 10^{-3}
 - b. 10^{-6}
 - c. 10^{-9}
 - d. 10^{-12}
20. 650 M Ω is equal to
- a. $6.50 \times 10^{-6} \Omega$
 - b. $650 \times 10^{-6} \Omega$
 - c. $6.50 \times 10^6 \Omega$
 - d. $650 \times 10^6 \Omega$
21. 35mV is equal to
- a. $3.5 \times 10^{-3} V$
 - b. $35 \times 10^{-3} V$
 - c. $3.5 \times 10^3 V$
 - d. $35 \times 10^3 V$
22. If you have a 6v battery and a 300 Ω resistor what current would flow through the circuit?
- a. 20 mA
 - b. 50 A
 - c. 294 A
 - d. 306 A
 - e. 1800 A
23. If you have a 100 Ω , 200 Ω and 200 Ω resistor in parallel the total resistance is
- a. 0 Ω
 - b. 50 Ω
 - c. 167 Ω
 - d. 500 Ω
24. If you have a 100 Ω , 200 Ω and 200 Ω resistor in series the total resistance is
- a. 0 Ω
 - b. 50 Ω
 - c. 167 Ω
 - d. 500 Ω

Figure 1

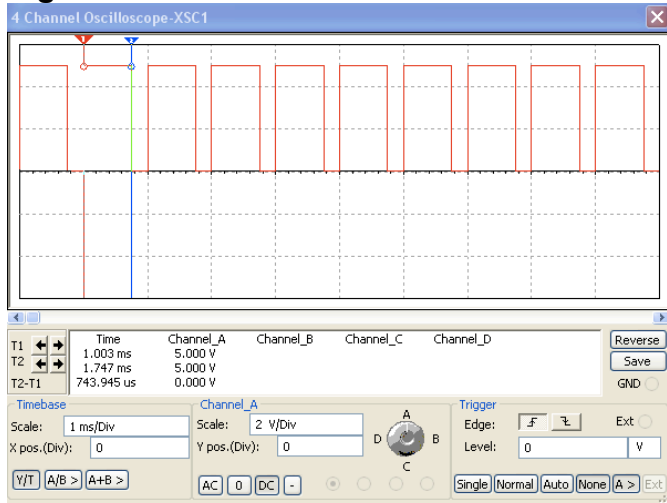

25. What is the amplitude

- a. 2 v
- b. .2 ms
- c. 5 v
- d. 1 ms

26. What is the period of the wave

- a. 1V
- b. 1ms
- c. 5V
- d. 5ms

27. What is the t_H

- a. .75 ms
- b. 1.00 ms
- c. 1.5 ms
- d. 1.75 ms

28. What is the Duty Cycle?

- a. 25%
- b. 50%
- c. 75%
- d. None of the above

29. You set up a 555 timer with $R_A=10k\Omega$, $R_B=15k\Omega$ and $C=260\mu F$. What is the Duty Cycle?

- a. 1.7%
- b. 2.6%
- c. 62.5%
- d. 66.7%


30. Which is not a subatomic particle?

- a. Proton
- b. Neutron
- c. Electron
- d. Potassium

31. Which element is not a good conductor

- a. Gold
- b. Silver
- c. Copper
- d. Phosphorus

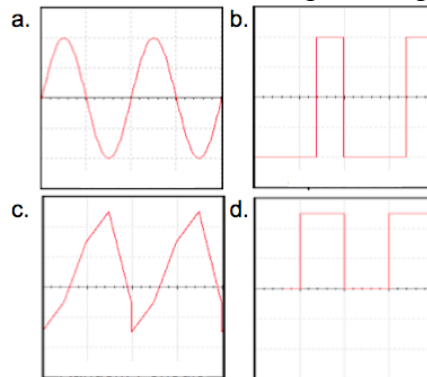
32. Which of the following is a digital wave



33. The main difference between combinational and sequential logic is

- a. Combinational requires a memory component
- b. Sequential requires a memory component
- c. Combinational has more than one input
- d. Sequential has more than one input

34. The circuit below is an example of a

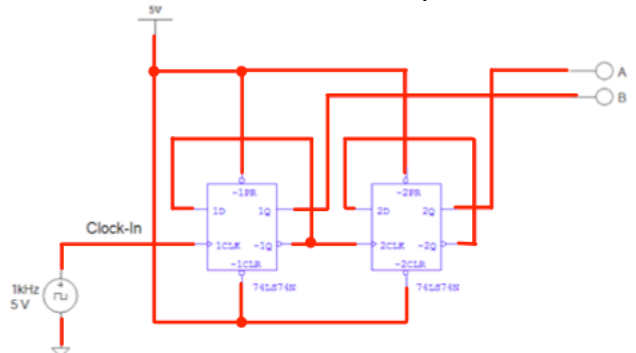

- a. 2-bit binary counter
- b. Divide by two
- c. Both a and b
- d. None of the above


35. This type of gate outputs a "1" when the input is "0"

- a. INVERT
- b. AND
- c. OR
- d. NOR

36. This type of gate outputs a “1” only when both inputs are a “0”
- INVERT
 - AND
 - NOR
 - NAND
37. This type of gate outputs a “0” When the inputs are “0” and “0”
- INVERT
 - XOR
 - NOR
 - NAND
38. This type of gate outputs a “1” when only one input is a “1”
- OR
 - NOR
 - XNOR
 - XOR
39. This type of gate outputs a “1” when both inputs are the same
- AND
 - NAND
 - XOR
 - XNOR
40. This type of gate outputs a “1” when both inputs are a “1”
- AND
 - NAND
 - NOR
 - INVERT
41. This type of gate outputs a “1” when any of the inputs are a “1”
- INVERT
 - AND
 - OR
 - XOR
42. This type of gate outputs a “1” if any inputs are a “0”
- NAND
 - NOR
 - XOR
 - XNOR

43. Rank the following from most gates found in an integrated circuit to least gates
- MSI>SSI>ULSI>GSI
 - GSI>ULSI>MSI>SSI
 - ULSI>GSI>SSI>MSI
 - SSI>MSI>GSI>ULSI
44. The 74LS08N IC we used in class is an example of
- GSI
 - LSI
 - MSI
 - SSI

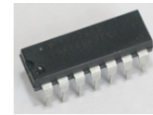45. What type of package is the following image



- DIP
- PLCC
- QFP
- SOIC

46. What type of package is the following image



- DIP
- PLCC
- QFP
- SOIC

47. Given the part number DM74ALS08N which segment tells you the manufacturer

- DM
- 74
- ALS
- 08
- N

48. Given the part number DM74ALS08N which segment tells you the package style

- DM
- 74
- ALS
- 08
- N

49. Given the part number DM74ALS08N which segment tells you the TTL type

- a. DM
- b. 74
- c. ALS
- d. 08
- e. N

50. Given the part number DM74ALS08N which segment tells you the logic function

- a. DM
- b. 74
- c. ALS
- d. 08
- e. N

51. Given the part number DM74ALS08N "ALS" means

- a. Automated low-power shottky
- b. Advanced low-power shottky
- c. American League Division Series
- d. Advanced Logic Series
- e. None of the above

Figure 2

Symbol	Parameter	Min	Nom	Max	Units
V _{CC}	Supply Voltage	4.75	5	5.25	V
V _{IH}	HIGH Level Input Voltage	2			V
V _{IL}	LOW Level Input Voltage			0.8	V
I _{OH}	HIGH Level Output Current			-0.4	mA
I _{OL}	LOW Level Output Current			8	mA
T _A	Free Air Operating Temperature	0		70	°C

52. Using Figure 2 what is the maximum voltage the IC can handle?

- a. 0 v
- b. .8 v
- c. 5.25 v
- d. Not enough information

53. In Figure 2 what is the lowest temperature the IC will function properly at?

- a. 0°C
- b. 70°C
- c. -.4mA
- d. 4.75v

Figure 3

Switching Characteristics

at V_{CC} = 5V and T_A = 25°C

Symbol	Parameter	R _L = 2 kΩ				Units
		C _L = 15 pF		C _L = 50 pF		
		Min	Max	Min	Max	
t _{PLH}	Propagation Delay Time LOW-to-HIGH Level Output	4	13	6	18	ns
t _{PLL}	Propagation Delay Time HIGH-to-LOW Level Output	3	11	5	18	ns

54. In Figure 3 what is the minimum high to low propagation delay time using a 50pF capacitor

- a. 3 ns
- b. 4 ns
- c. 5 ns
- d. 6 ns

55. What is 29₁₀ in binary?

- a. 01000₂
- b. 10111₂
- c. 11101₂
- d. None of the above

56. What is 29₁₀ in octal-decimal?

- a. 35₈
- b. 53₈
- c. 3 101₈
- d. 101 3₈

57. What is 29₁₀ in hexadecimal?

- a. C1_H
- b. 1C_H
- c. 13_H
- d. 113_H

58. What is 11111₂ in base 10?

- a. 11111₁₀
- b. 31₁₀
- c. 62₁₀
- d. 63₁₀

59. What is 11011₂ in octal-decimal?

- a. 27₈
- b. 33₈
- c. B1₈
- d. 1B₈

60. What is 110111₂ in hexadecimal?

- a. 27_H
- b. 33_H
- c. 37_H
- d. B7_H

Figure 4

X	Y	Z	F ₃
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

61. Which is NOT a min-term for Figure 4

- a. 001
- b. 011
- c. 101
- d. All of the above
- e. None of the above

62. Which is NOT a min-term for Figure 4

- a. $\overline{X}YZ$
- b. $X\overline{Y}Z$
- c. XYZ
- d. All of the above
- e. None of the above

63. F₄ is written in

$$F_4 = (W + \overline{X} + \overline{Y} + Z)(\overline{W} + X + \overline{Y})(W + \overline{Z})$$


- a. SPO logic
- b. POS logic
- c. SOP logic
- d. PSO logic

64. F₂ is written in

$$F_2 = \overline{A}B\overline{C}D + B\overline{C}D + A\overline{B}$$


- a. SPO logic
- b. POS logic
- c. SOP logic
- d. PSO logic

65. The following circuit is designed in

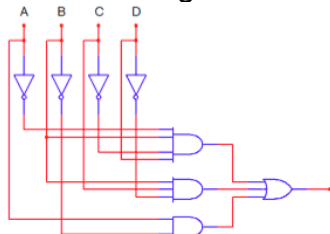


- a. SPO logic
- b. POS logic
- c. SOP logic
- d. PSO logic

66. The following circuit is designed in

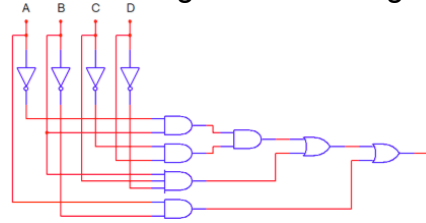

- a. SPO logic
- b. POS logic
- c. SOP logic
- d. PSO logic

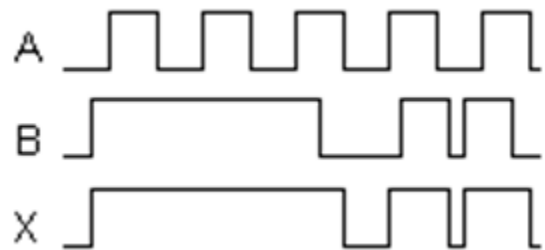67. The following waveform pattern with A and B are inputs, X is the output, is for a(n)



- a. 2-input AND gate
- b. 2-input OR gate
- c. 2-input XOR gate
- d. 2-input XNOR gate
- e. 2-input NAND gate

68. The equivalent to the following diagram is



- a. AND
- b. OR
- c. INVERT
- d. None of the above

69. The equivalent to the following diagram is



- a. AND
- b. OR
- c. INVERT
- d. None of the above

70. The equivalent to the following diagram is




- a. AND
- b. OR
- c. INVERT
- d. None of the above

71. The equivalent to the following diagram is




- a. AND
- b. OR
- c. INVERT
- d. None of the above

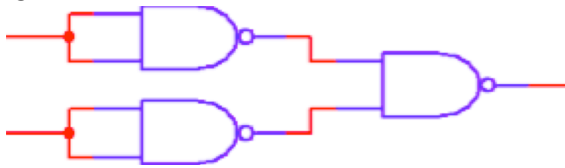72. The equivalent to the following diagram is




- a. AND
- b. OR
- c. INVERT
- d. None of the above

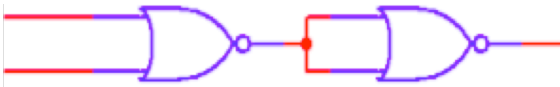73. The equivalent to the following diagram is



- a. AND
- b. OR
- c. INVERT
- d. None of the above

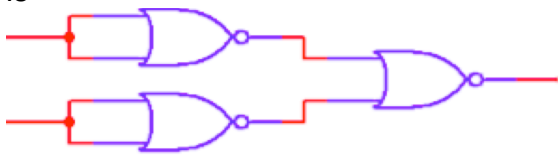74. The equivalent to the following diagram is



- a. AND
- b. OR
- c. INVERT
- d. None of the above

75. Which segments are not turned on for a seven segment display showing



- a. a and b
- b. a and d
- c. b and e
- d. c and f

76. What is the top of the following common cathode display connected to?



- a. Ground
- b. VCC
- c. Resistor
- d. None of the above

77. Solve the following binary addition problem

$$\begin{array}{r} 01001_2 \\ + 00011_2 \\ \hline \end{array}$$

- a. 01000
- b. 01100
- c. 01110
- d. 01111

78. Solve the following binary addition problem

$$\begin{array}{r} 01011_2 \\ + 00011_2 \\ \hline \end{array}$$

- a. 01000₂
- b. 01100₂
- c. 01110₂
- d. 01111₂

79. What is the two's complement of (-7) in 4-bit binary?

- a. 0111_2
- b. 1000_2
- c. 1001_2
- d. 1100_2

80. In two's complement 8-bit binary what is the largest positive value?

- a. 127_{10}
- b. 128_{10}
- c. 255_{10}
- d. 256_{10}

81. In two's complement 8-bit binary what is the largest negative value?


- a. -127_{10}
- b. -128_{10}
- c. -255_{10}
- d. -256_{10}

82. In two's complement 8-bit binary what is the answer to

$$\begin{array}{r} 01001011_2 \\ + 11100011_2 \\ \hline \end{array}$$

- a. 100101110_2
- b. 001011110_2
- c. 1001011100_2
- d. 00101010_2

Figure 5

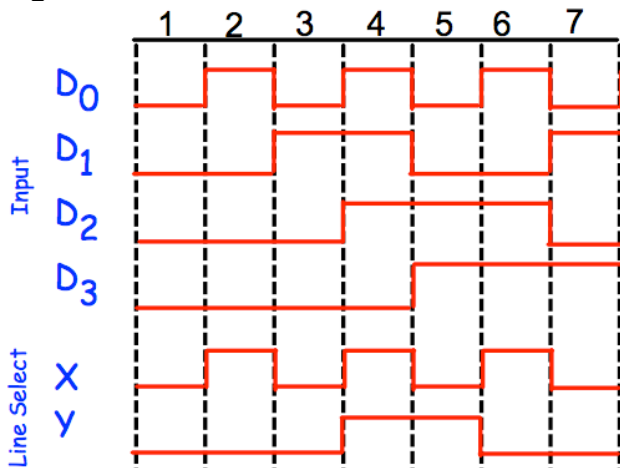

83. Figure 5 is showing the Input and Line Select for a

- a. Multiplexer
- b. De-multiplexer
- c. Divide by two circuit
- d. RC circuit

84. In Figure 5 the output at point 3 is equal to

- a. D_0
- b. D_1
- c. D_2
- d. D_3

85. In Figure 5 the output at point 5 is equal to

- a. D_0
- b. D_1
- c. D_2
- d. D_3


86. A De-multiplexer function is to manage

- a. 1 input into multiple outputs
- b. Multiple inputs into 1 output
- c. Count in binary
- d. None of the above

87. A Multiplexer function is to manage

- a. 1 input into multiple outputs
- b. Multiple inputs into 1 output
- c. Count in binary
- d. None of the above

Figure 6

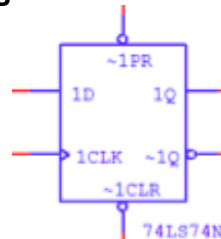

88. What is the component in Figure 6

- a. D Flip-Flop
- b. De-Multiplexer
- c. Multiplexer
- d. Resistor Pack

89. If a low input is put into the Preset of Figure 6 the Q is

- a. Depends on the input
- b. Depends on the previous output
- c. Always 1
- d. Always 0

90. If a low input is put into the Clear of Figure 6 Flop the Q is

- a. Depends on the input
- b. Depends on the previous output
- c. Always 1
- d. Always 0

Free Response

1. Create a divide by 2 circuit connected to a second divide by two circuit using D-Flip Flops. (4pts)

1. Use a K-Map to determine the simplest expression given the following truth table. (3pts)

X	Y	Z	F ₂
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	X
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	X

2. Create a truth table for

$$F_3 = X + YZ + \overline{X}\overline{Y}\overline{Z} \text{ (2pts)}$$

X	Y	Z	F ₃
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

3. Show step by step the Boolean simplification for $F_4 = WWX + \overline{W} + \overline{Z} + Y\overline{Y}Z + \overline{\overline{X}\overline{Y}\overline{Z}}$ (4pts)

4. Your teacher keeps their finals in their office that is protected by an alarm that goes off if, the door is opened without a key or if the window is opened.

Key: 1= key used/0=key not used

Door: 1=door closed/0=door open

Window: 1=window closed/0=window open

- a. Create a Truth Table (4pts)
- b. Create a K-map (3pts)
- c. Derive the simplest logic expression (2pts)
- d. Implement the circuit with NAND gates (3pts)


Answer Key

MC

1. C	31. D	61. E
2. C	32. D	62. C
3. D	33. B	63. B
4. B	34. C	64. C
5. A	35. A	65. C
6. D	36. B	66. B
7. D	37. B	67. B
8. C	38. D	68. C
9. C	39. D	69. A
10. C	40. A	70. C
11. C	41. C	71. D
12. D	42. B	72. B
13. E	43. B	73. B
14. A	44. D	74. A
15. C	45. A	75. B
16. C	46. D	76. A
17. C	47. A	77. B
18. B	48. E	78. C
19. D	49. B	79. C
20. D	50. D	80. A
21. B	51. B	81. B
22. A	52. C	82. B
23. B	53. B	83. A
24. D	54. B	84. A
25. C	55. C	85. B
26. B	56. A	86. A
27. A	57. A	87. B
28. C	58. B	88. A
29. C	59. B	89. C
30. D	60. C	90. D

Free Response

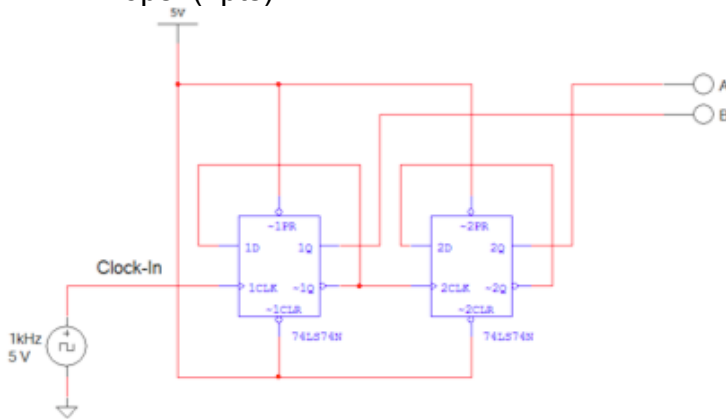2. Create a divide by 2 circuit connected to a second divide by two circuit using D-Flip Flops. (4pts)



3. Use a K-Map to determine the simplest expression given the following truth table. (3pts)

X	Y	Z	F ₂
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	X
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	X

$F_2 = XY + Z$

	\bar{Z}	Z
$\bar{X}\bar{Y}$	0 0	1 1
$\bar{X}Y$	0 2	X 3
XY	1 6	X 7
$X\bar{Y}$	0 4	1 5

4. Create a truth table for

$F_3 = X + YZ + \bar{X}\bar{Y}\bar{Z}$ (2pts)

X	Y	Z	F ₃
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

5. Show step by step the Boolean simplification for $F_4 = WWX + \bar{W} + \bar{Z} + Y\bar{Y}Z + \bar{X}\bar{Y}\bar{Z}$ (4pts)

$F_4 = WX + \bar{W} + \bar{Z} + Y\bar{Y}Z + \bar{X}\bar{Y}\bar{Z}$

$F_4 = WX + \bar{W}\bar{Z} + Y\bar{Y}Z + \bar{X}\bar{Y}\bar{Z}$

$F_4 = WX + \bar{W}\bar{Z} + 0Z + \bar{X}\bar{Y}\bar{Z}$

$F_4 = WX + \bar{W}\bar{Z} + 0 + \bar{X}\bar{Y}\bar{Z}$

$F_4 = WX + \bar{W}\bar{Z} + 0 + (\bar{X} + \bar{Y})\bar{Z}$

$F_4 = WX + \bar{W}\bar{Z} + 0 + (X + Y)\bar{Z}$

$F_4 = WX + \bar{W}\bar{Z} + 0 + X\bar{Z} + Y\bar{Z}$

$F_4 = WX + \bar{W}\bar{Z} + X\bar{Z} + Y\bar{Z}$

6. Your teacher keeps their finals in their office that is protected by an alarm that goes off if, the door is opened without a key or if the window is opened.

Key: 1= key used/0=key not used

Door: 1=door closed/0=door open

Window: 1=window closed/0=window open

- Create a Truth Table (4pts)
- Create a K-map (3pts)
- Derive the simplest logic expression (2pts)
- Implement the circuit with NAND gates (3pts)

K	D	W	F _A
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

	\overline{W}	W
$\overline{K}\overline{D}$	1 0	1 1
$\overline{K}D$	1 2	0 3
$K\overline{D}$	1 6	0 7
KD	1 4	0 5

$$F_A = \overline{K}\overline{D} + \overline{W}$$

Simplified NAND

